

1st order circuit and Inductors

Monday, March 11, 2019 2:42 PM

- 1st- order circuit: Circuit whose voltages and currents are described by 1st order

Differential equation.

- RL circuits

$$V_L = L \frac{di}{dt}$$

- RC circuits

$$i_C = C \frac{dV}{dt}$$

- Response: Currents and voltages that arise when energy is acquired or released

by a circuit


- Natural Response: No external sources

- Step Response: Sudden application of DC current or voltage

- Under DC sources

- Transient state

- Steady-state

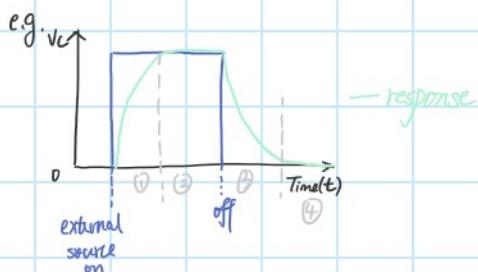

Step response ①, ②

Natural response ②, ③

Transient state ①, ②

Steady state ②, ④

e.g. Natural Response under RL circuit

Switch is open at $t=0$.

$$L \cdot \frac{di}{dt} + R i = 0$$



- initial response $i(0)$.

$$L \frac{di}{dt} + RI = 0$$

$$\frac{di}{t} = -\frac{R}{L} dt$$

$$i(t) = -\frac{R}{L} t + C$$


$$i(t) = I_0 e^{-\frac{R}{L} t} = I_0 e^{-\frac{R}{L} t}$$

$$i_L(0^+) = i_S = I_0 \quad (\text{Inductors do not allow instantaneous changes in } i)$$

∴ natural response $= i(t) = I_0 e^{-\frac{R}{L} t}$

$$v(t) = i(t) \cdot R = I_0 R e^{-\frac{R}{L} t}$$

$$v(0^-) = 0, v(0^+) = I_0 R = I_0 R$$

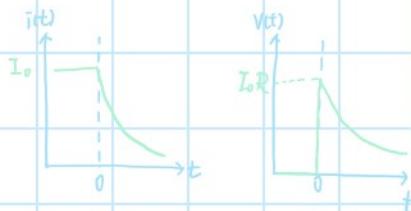

D. the instant when the switch is open

when $i_S = 1A, R = 10\Omega, L = 1mH$

$$i(t) = I_0 e^{-\frac{R}{L} t} = e^{-10000t} A, t > 0$$

$$v(t) = R I_0 e^{-10000t} = 10 e^{-10000t} V$$

- $i(t) = I_0 e^{-\frac{R}{L} t}$ for $R-L$ circuit.


time constant $\tau = \frac{L}{R}$ $i(t) = I_0 e^{-\frac{t}{\tau}}$ (natural response)

$$\frac{di}{dt} = -\frac{I_0}{\tau} e^{-\frac{t}{\tau}} \Rightarrow \frac{di}{dt}(0^+) = -\frac{I_0}{\tau} \quad (\text{slope at } t=0)$$

tangent: $i_f(t) = i_0 - \frac{i_0}{\tau} t$


$$i_0(t) = 0, t = \tau$$

$$t = \tau, i(t) = 0.37 I_0$$

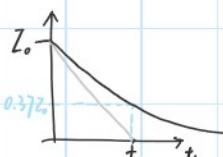

$t=5\tau, i(t) < 0.01 I_0 \rightarrow$ steady state

- Power & Energy

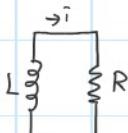

Power dissipated in R

$$P = V_i = i^2 R = I_0^2 R e^{-\frac{2t}{\tau}} \quad t > 0$$

Energy dissipated in R

$$W_R = \int_{-\infty}^t I_0^2 R e^{-\frac{2t}{\tau}} dt = -\frac{1}{2} I_0^2 R e^{-\frac{2t}{\tau}} \Big|_{-\infty}^t = \frac{1}{2} I_0^2 R t (1 - e^{-\frac{2t}{\tau}})$$

Energy dissipated in R

$$W_R = \int_0^t I_o^2 R e^{-\frac{Rt}{L}} dt = -\frac{I_o^2 R}{2} e^{-\frac{Rt}{L}} \Big|_0^t = \frac{1}{2} L I_o^2 (1 - e^{-\frac{Rt}{L}})$$

Energy delivered by L


$$\Delta W_L = W_L(t) - W_L(0) = \frac{1}{2} L i^2(t) - \frac{1}{2} L i^2(0)$$

$$= \frac{1}{2} L I_o^2 (e^{-\frac{Rt}{L}} - 1)$$

e.g. Calculate $i(t)$. (Switch open from $t=0$)


$\bar{I}=0$, L behave like a wire
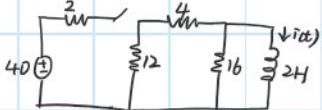
$$\bar{i}(t) = \frac{40}{2 + (12//4)} = \frac{40}{5} = 8A$$



$$i(t) = 8 \cdot \frac{12}{2+4} = 6A, \quad \bar{i}(0) = \bar{i}(0^-) = 6A$$

$t > 0$

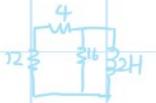

$$R_{eq} = 16//16 = 8\Omega$$



$$\therefore \bar{i} = 6e^{-\frac{Rt}{L}}$$

Response of RC circuits

Wednesday, March 13, 2019 2:53 PM

- $V(t) = V_0 e^{-\frac{t}{RC}}$ unit: V $t \geq 0$, $V_0 = V$

$$T = RC \text{ unit: } s^{-1}$$

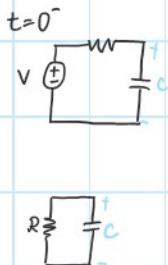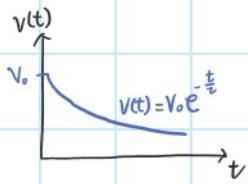

- $i(t) = \frac{V(t)}{R} = \frac{V_0}{R} e^{-\frac{t}{T}}$ for $t > 0$

- Power & Energy in the resistor

- Power dissipated by R.

$$P = V_i = \frac{V_0^2}{R} e^{-\frac{2t}{T}}, t > 0^+$$

- Energy dissipated by R:

$$W_R = \int_0^t P dt = \int_0^t \frac{V_0^2}{R} e^{-\frac{2t}{T}} dt = \frac{1}{2} C V_0^2 (1 - e^{-\frac{2t}{T}})$$

Energy change by C:

$$\Delta W_C = W_C(t) - W_C(0) = \frac{1}{2} C V_0^2 (e^{-\frac{2t}{T}} - 1)$$

- $t \rightarrow \infty$, $V_C \rightarrow 0$, when fully charged, C acts like short circuit.

e.g. $V_C(0) = 60V$. find $V_C(t)$, $V_x(t)$, $i_o(t)$ for $t > 0$


$$Req = (12//6) + 8 = 4 + 8 = 12\Omega$$

$$Z = RC = 12 \times \frac{1}{3} = 4$$

$$V_C(t) = 60 e^{-0.25t} V$$

$$V_x(t) = V_C(t) \cdot \frac{12//6}{12} = 20 e^{-0.25t}$$

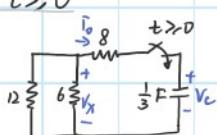
$$i_o(t) = C \cdot \frac{dV_C}{dt} = -\frac{V_C}{12}$$



- Step response of R-C

- $V_C(t) = V_s + (V_0 - V_s)e^{-\frac{t}{T}}$, $T = RC$

V_0 : initial voltage

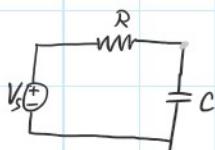

$$V(t) = V_s + (V_0 - V_s)e^{-\frac{t}{RC}}$$



V_0 : initial voltage

$$\frac{V_s(t) - V_s}{R} + C \frac{dV}{dt} = 0$$

$$\frac{dV_c}{V_c - V_s} = -\frac{1}{RC} dt \rightarrow \int_{V_0}^{V_c(t)} \frac{dV}{V - V_s} = -\frac{1}{RC} \int_0^t dy$$

$$V_c(t) = V_s + (V_0 - V_s)e^{-\frac{t}{RC}} = V_s + (V_0 - V_s)e^{-\frac{t}{T}}, T = RC$$

$$I_o = \frac{V_s - V_0}{R}, i(\infty) = 0$$

$$i(t) = \frac{V_s - V_0}{R} e^{-\frac{t}{T}}$$

Step Response of RL

Friday, March 15, 2019 2:45 PM

$$I_{lt} = \frac{V_s}{R} + (I_o - \frac{V_s}{R}) e^{-\frac{Rt}{L}} = \frac{V_s}{R} + (I_o - \frac{V_s}{R}) e^{-\frac{t}{\tau}}$$


$$V_L = (V_s - I_o R) e^{-\frac{t}{\tau}}$$

e.g. Assume that the switch in the circuit has been in position b for a long time and at $t=0$ it moves to position a.

Find (a) $i(0^+)$; (b) $v(0^+)$; (c) τ ; (d) $i(t)$, $t > 0$; (e) $v(t)$, $t > 0^+$

(a) inductor acts as short.

$$i(0^-) = \frac{24A}{2\Omega} = 12A$$

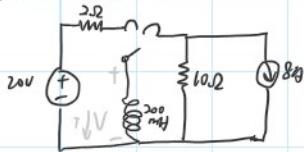

(b)



$$V(0^+) = -10(8+12) = -200V$$

$$(c) \tau = 20ms = \frac{200m}{10\Omega} = 20ms$$

$$(d) \bar{i}(t) = i_f + [i(0^+) - i_f] e^{-\frac{t}{\tau}}, \quad i_f = -8A$$

$$i(t) = -8 + 20e^{-50t} A$$

$$(e) v(t) = L \cdot \frac{di}{dt} = -200e^{-50t}$$

General Solutions for Natural and Step Response

Natural Response



Step Response



Equation (describe both)

$$Ri + L \frac{di}{dt} = V_s \quad \frac{1}{R}v + C \frac{dv}{dt} = I_s$$

$$\frac{1}{\tau}i + \frac{di}{dt} = \frac{V_s}{L} \quad \frac{1}{\tau}v + \frac{dv}{dt} = \frac{I_s}{C}$$

Time constant

$$\tau = L/R$$

$$\tau = RC$$

$t \rightarrow \infty$

$$i(\infty) = V_s/R = I_s$$

$$v(\infty) = I_s R = V_s$$

20

- All equations are of the form $\frac{dx}{dt} + \frac{1}{\tau}x = K$

o τ : time constant K : constant

- final steady state is reached with $\frac{dx_f}{dt} = 0 \Rightarrow x_f = K\tau$

- final steady state is reached with $\frac{dx_f}{dt} = 0 \rightarrow x_f = K C$

$x(t)$ changes exponentially from $x(t_0)$ to x_f at time constant τ

$\rightarrow x(t) \text{ contains } (x(t_0) - x_f) e^{-\frac{t-t_0}{\tau}}$

$$x(t) = x(\infty) + (x(t_0) - x(\infty)) e^{-\frac{t-t_0}{\tau}}$$

Sequential Switching

Friday, March 15, 2019 3:12 PM


- Where there're more than one switching operation.

e.g. Switch move to 2 at $t=0$ (previous 1). Then return to 1 at $t=4s$.

find $V_c(t)$, $t \geq 0$

$$t \in [0, 4], V_c(\infty) = 10$$
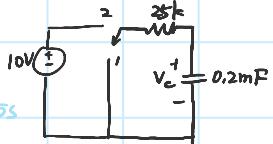
$$V_c(0) = 0, \tau = 25k \times 0.2m = 5s$$



$$V_c(t) = 10(1 - e^{-\frac{t}{\tau}})$$

$$(V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{-0.2t})$$

$t > 4$


$$V_c(4) = 10(1 - e^{-0.8t}) = 5.5, V_c(\infty) = 0$$

$$V_c(t) = 5.5 e^{\frac{t}{5}}$$

Prob

Monday, March 18, 2019 12:57 AM

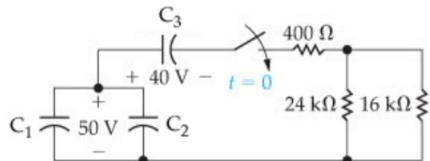At the time the switch is closed in the circuit in (Figure 1), the voltage across the paralleled capacitors is 50 V and the voltage on the C_3 capacitor is 40 V. Take that $C_1 = 470 \text{ nF}$, $C_2 = 970 \text{ nF}$ and $C_3 = 510 \text{ nF}$.



What percentage of the initial energy stored in the three capacitors is dissipated in the $24 \text{ k}\Omega$ resistor?

Express your answer using two decimal places.

► **View Available Hint(s)**

$$\% \text{ diss} = 0.33 \%$$

What percentage of the initial energy stored in the three capacitors is dissipated in the 400Ω resistor?

Express your answer using two decimal places.

► **View Available Hint(s)**

$$\% \text{ diss} = 0.03 \%$$

Part A.

$$E_{\text{tot}} = \frac{1}{2}(C_1 + C_2)50^2 + \frac{1}{2}C_340^2 = 2.208 \times 10^{-3} \text{ J}$$

$$C_{\text{eq}} = \frac{(470+970) \times 510}{470+970+510} = 376.6 \times 10^{-9} \text{ F}$$

$$R_{\text{eq}} = 9.6 + 0.4 = 10 \text{ k}\Omega$$

$$V_{\text{eq}} = 50 - 40 = 10 \text{ V}$$

$$V(t) = 10 e^{-266t}$$

$$i_{24k}(t) = 376.6 \times 10^{-9} \times (-266) \times 10 e^{-266t} \times \frac{16}{16+24} = 4 \times 10^{-4} e^{-266t}$$

$$P = i_{24k}^2 R = 10^{-8} \times 24 \times 10^3 e^{-532t} = 3.84 \times 10^{-3} e^{-532t}$$

$$W_{24k} = \int_0^\infty P dt = \frac{24 \times 10^3}{-532} e^0 = \frac{7.2 \times 10^{-6}}{4.15 \times 10^{-5}}$$

$$\frac{W_{24k}}{E_{\text{tot}}} \% = \frac{7.2 \times 10^{-6}}{2.208 \times 10^{-3}} \times 100 = 0.33\%$$

B.

$$i_{400} = 10^{-3} e^{-266t}$$

$$i^2 R = 10^{-6} \times 400 e^{-532t} = 4 \times 10^{-10} e^{-532t}$$

$$W_{400} = \int_0^\infty 4 \times 10^{-10} e^{-532t} dt = \frac{4 \times 10^{-10}}{-532} = 7.52 \times 10^{-7} J$$

$$\frac{W_{400}}{E_{tot}} = \frac{7.52 \times 10^{-7}}{2.208 \times 10^{-6}} \times 100 = 0.03\%$$

C.

$$i_{16k} = 10^{-3} e^{-266t} + \frac{24}{24+16} = 6 \times 10^{-4} e^{-266t}$$

$$i^2 R = 3.6 \times 10^{-7} e^{-532t} + 16 \times 10^{-3} = 5.76 \times 10^{-3} e^{-532t} W$$

$$W_{16k} = \int_0^\infty 5.76 \times 10^{-3} e^{-532t} dt = \frac{5.76 \times 10^{-3}}{-532} = 1.08 \times 10^{-5} J$$

$$\frac{W_{16k}}{E_{tot}} = \frac{1.08 \times 10^{-5}}{2.208 \times 10^{-6}} \times 100 = 0.49\%$$


D. $| -0.49\% - 0.33\% - 0.03\% | = 0.9915 = 99.15\%$

■ Review | Constants

The switch in the circuit seen in the figure has been in position x for a long time. At $t = 0$, the switch moves instantaneously to position y. (Figure 1)

Figure

1 of 1

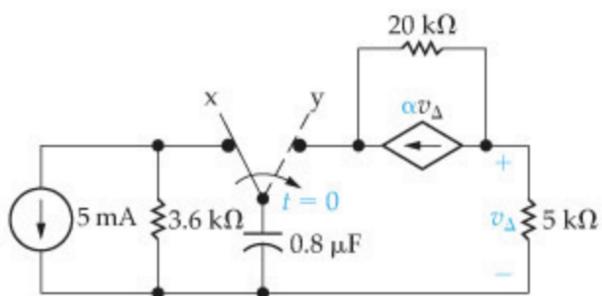

Part A

Find α so that the time constant for $t > 0$ is 40 ms.

Express your answer to three significant figures and include the appropriate units.

$$\alpha = 2.50 \times 10^{-4} \frac{A}{V}$$

[Submit](#)

[Previous Answers](#)

Correct

Part B


For the found α , find v_Δ .

Express your answer in volts in terms of t , where t is in seconds.

$$v_\Delta = -\frac{9}{5} e^{-\frac{t}{4 \cdot 10^{-2}}} V$$

[Submit](#)

[Previous Answers](#)

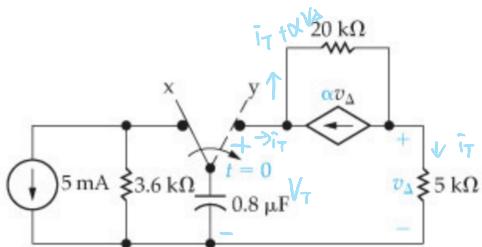

A.

$$\begin{cases} V_T = 20k(\bar{i}_T + \alpha V_\Delta) + 5k\bar{i}_T \\ V_\Delta = 5k\bar{i}_T \end{cases}$$

$$\therefore V_T = 25k\bar{i}_T + \alpha 10^2 k\bar{i}_T$$

$$\therefore R_{Th} = \frac{V_T}{\bar{i}_T} = 25k + \alpha 100k$$

$$R_{Th} \cdot C = 4 \times 10^{-2}$$

$$R_{Th} = 25k + \alpha 100k^2 = 50k$$

$$\alpha = \frac{25k}{100k^2} = 2.5 \times 10^{-4} A/V$$



$$V_o = 18V$$

$$V_o(t) = 18 e^{-\frac{t}{40m}}$$

$$V_\Delta = -18 \times \frac{5}{50} e^{-\frac{t}{40m}}$$