

6.1 Inductance, Capacitance, and Mutual Inductance

Wednesday, February 27, 2019

2:52 PM

- Inductors & Capacitors


- Passive circuit elements, cannot generate energy (like resistor)

- can store/deliver energy that was previously stored.

- Energy stored

- Inductor: electromagnetic field, created by moving charge.

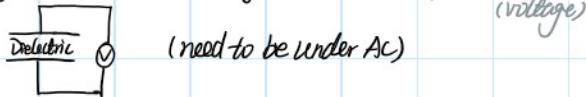- Capacitor: electrostatic field, created by displaced charges.



- Inductor

- Unit: Tesla (T)

$$\frac{L}{V}$$

→

- $V = L \cdot \frac{di}{dt}$

- Current is constant: $V=0$, just like a short circuit.

- Current can only change gradually.

otherwise $V \rightarrow \infty \Rightarrow$ An inductor "opposes" any change in current.

Voltage can change instantaneously.

- $i = \frac{1}{L} \int_{t_0}^t V dt + i(t_0)$ Remember L , $i(t_0)$!

$$V dt = L \cdot di \Rightarrow \int_{t_0}^t V dt = L \int_{i(t_0)}^{i(t)} di$$
$$= L(i(t) - i(t_0))$$


$$\therefore i(t) = \frac{1}{L} \int_{t_0}^t V dt + i(t_0)$$

$$t_0 = 0 \rightarrow i(t) = \frac{1}{L} \int_0^t V dt + i(0)$$

- $V(t)$ will change polarity if change the sign of slope of i .

e.g. $V = \begin{cases} 0 & t < 0 \\ 20te^{-10t} & t \geq 0 \end{cases}$, $L = 100 \text{ mH}$, $i(t) ?$
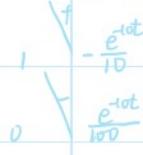
$$\begin{aligned} \bar{i}(t) &= \frac{1}{L} \int_0^t 20te^{-10t} dt + 0 \\ &= \left(-\frac{te^{-10t}}{10} - \frac{e^{-10t}}{100} + \frac{1}{100} \right) * 200 \quad t \quad e^{-10t} \\ &= -20te^{-10t} - 2e^{-10t} + 2 \end{aligned}$$



- Power & Energy in the inductor

$P = L \cdot \bar{i} \cdot \frac{di}{dt} = V = V \cdot \left(\frac{1}{L} \int_{t_0}^t V dt + \bar{i}(t_0) \right)$

Energy: $W = \frac{1}{2} \bar{i}^2$ • Remember that $W_{eq} \neq \sum W_i$, because some energy will be trapped in L_s .

$$P = \frac{dW}{dt} = L \frac{di}{dt} \quad \therefore dW = L i di \quad W = \int_0^t L y dy = \frac{L^2}{2}$$

e.g. $V(t) = \begin{cases} 0, t < 0 \\ 5V, t \geq 0 \end{cases}, \quad i(0) = 0, \quad L = 100 \text{ mH}$

(a) Current $i(t)$?

(b) $p(t), w(t)$?

(c) does i, p, w become 0 if shut down V at $t = 10$?

(a) $\bar{i} = \frac{1}{L} \int_0^t 5 dt + 0 = 5t \times 10 = 50t \text{ (A)}, \quad t > 0$

(b) $p(t) = V \cdot \bar{i} = 5 \cdot 50t = 250t \text{ (W)}$

two soln { $w(t) = \frac{1}{2} \cdot L \bar{i}^2 = \frac{1}{2} \cdot 2500t^2 \cdot 0.1 = 125t^2 \text{ (J)}$

$$w(t) = \int_0^t P dt + w(0) = 125t^2 \text{ (J)}$$

(c) $p(t) = V \bar{i} = 0$

\bar{i}, w doesn't go to 0 immediately.

$$\bar{i} = \frac{1}{L} \int_0^{10} V dt + \frac{1}{L} \int_{10}^t V dt = 500 + 0 = 500 \text{ (A)}$$

$$w = \int_0^{10} P dt + \int_{10}^t P dt = 125 \times 10^2 = 1.25 \times 10^4 \text{ (J)}$$

- Inductors in series $L_{eq} = \sum_{i=1}^n L_i$

$$V_j = L_j \cdot \frac{di}{dt} \Rightarrow V_{tot} = \sum_{j=1}^n L_j \frac{di}{dt}$$

$$L_{eq} = \sum L_j$$

- Inductors in parallel $\frac{1}{L_{eq}} = \sum_{i=1}^n \frac{1}{L_i}$

$$\bar{i}_j = \frac{1}{L_j} \int_{t_0}^t V dt + i_j(0)$$

$$\bar{i}_{tot} = \sum_{j=1}^n \frac{1}{L_j} \int_{t_0}^t V dt + i_j(0)$$

$$\hat{i}_{\text{tot}} = \sum_{j=1}^n \frac{1}{L_j} \int_{t_0}^t v dt + j(t_0)$$
$$= \hat{i}_{\text{tot}} = \left(\int_{t_0}^t v dt + \cdot \sum_{j=1}^n \frac{1}{L_j} \right)$$
$$\hat{i}(t_0) = \sum_{j=1}^n \hat{i}_j(t_0)$$

Capacitance

Tuesday, March 5, 2019

9:01 AM

- Capacitor: Consists of two conductors separated by an insulator or dielectric material. Unit: Farad (F)

$$C = \frac{\epsilon A}{d}$$

$$\epsilon = \epsilon_r \epsilon_0 \quad \begin{matrix} \text{relative permittivity} \\ \text{permittivity of dielectric} \end{matrix}$$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m} \quad \text{Electrical permittivity of free space}$$

$$q = CV \quad \begin{matrix} \text{charge stored in the capacitor} \\ \text{voltage} \end{matrix}$$

- practical range: pF to μF



Displacement current



$$i = \frac{dq}{dt} = \frac{d(CV)}{dt} = C \frac{dv}{dt}$$

- If v is a constant, $i=0$

(if DC, $i=0$)

- v cannot change instantaneously, or $i \rightarrow \infty$

but i can.

$$V(t) = \frac{1}{C} \int_{t_0}^t i dt + V(t_0)$$

$$i = C \frac{dv}{dt}$$

$$idt = CdV$$

$$V(t) - V(t_0) = \frac{1}{C} \int_{t_0}^t idt$$

$$V(t) = \frac{1}{C} \int_{t_0}^t idt + V(t_0)$$

- $V(t)$ and $i(t)$ doesn't come to max at the same time

- when $\frac{dv}{dt}$ change sign, $i(t)$ change its sign.

- Power $P = vi = Cv \frac{dv}{dt}$ or $P = \frac{i}{C} \left(\int_{t_0}^t idt + V(t_0) \right)$

$$\text{Energy } W = \frac{1}{2} CV^2$$

$$P = \frac{dw}{dt}$$

$$\text{Energy } W = \frac{1}{2} CV^2 \quad P = \frac{dW}{dt}$$

$$Pdt = dW$$

$$W = \frac{1}{2} CV^2$$

$$\text{e.g. } C = 1\text{ mF}, \quad i(t) = \begin{cases} 0, & t < 0 \\ 1\text{ mA}, & 0 \leq t \leq 10\text{s} \\ 0, & t > 10\text{s} \end{cases}, \quad v(0) = 0$$

(1) find $v(t)$

(2) $P(t), W(t)$

$$(1) \quad v(t) = \int_0^t i(t) dt + 0 \\ = t, \quad t \in [0, 10]$$

$$v(t) = \int_0^{10} i(t) dt + 0 \\ = 10, \quad t \in [10, +\infty)$$


$$(2) \quad P = iV = 10t, \quad t \in [0, 10]$$

$$P = iV = 0, \quad t \in (10, +\infty)$$

$$W = \frac{1}{2} CV^2 = \frac{1}{2} Ct^2 \quad t \in [0, 10]$$

$$W = \frac{100}{2} C = 50 \times 10^{-3} = 5 \times 10^{-2} \text{ J}, \quad t \in (10, +\infty)$$

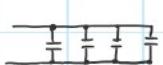- Capacitors in Parallel $C_{eq} = \sum C_i$



$$\bar{i}_i = C_i \frac{dv}{dt}$$

$$i_{tot} = \sum \bar{i}_i = \frac{dv}{dt} \sum C_i$$

$$\therefore C_{eq} = \sum C_i$$

- Capacitors in Series $\frac{1}{C_{eq}} = \sum \frac{1}{C_i}$



$$\bar{i} = \bar{i}_i = C_i \frac{dV_i}{dt}$$

$$V_i = \frac{1}{C_i} \left[\int_{t_0}^t \bar{i} dt + V(0) \right]$$

$$V = \sum V_i = \sum \frac{1}{C_i} \cdot \left(\int_{t_0}^t idz + V(0) \right)$$


$$\frac{1}{C_{eq}} = \sum \frac{1}{C_i}$$

- Voltage division with Capacitors

$$q_1 = q_2$$



$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

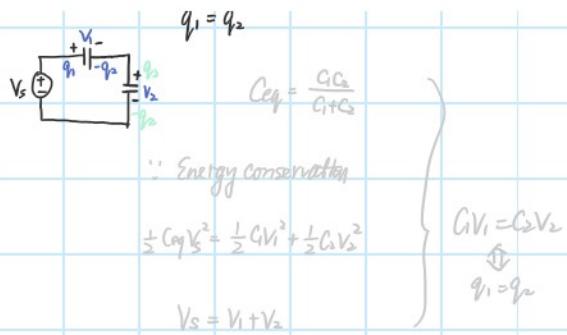


$\circ V_1 = \frac{C_2}{C_1 + C_2} V_s, \quad V_2 = \frac{C_1}{C_1 + C_2} V_s$

$$V_2 = V_s - V_1 \quad V_2 C_2 = C_1 (V_s - V_1)$$

(AP. 6.5 doesn't obey $C_1 V_1 = C_2 V_2$, the wire is not neutral)

So can't use $\frac{1}{2} C_{eq} V_s^2 = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2$

- Determine C_{ab} and V_{ab} at ab

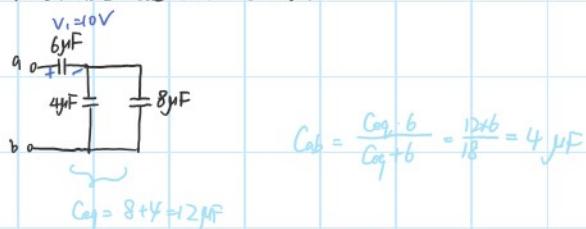

$$C_1 V_1 = C_{eq} V_{eq}$$

$$V_{eq} = \frac{a}{C_{eq}} \cdot V_s$$

$$V_{ab} = V_{eq} + V_1 = \frac{a + C_1}{C_{eq}} V_s = \frac{6 + 2}{12} \cdot 10 = 15V$$



e.g. DRAM (Dynamic Random Access Memory)

- 1-bit memory storage:

$$V_{cell} > 1.5V \text{ true(1)}$$

$$V_{cell} < 1.5V \text{ false(0)}$$

- The switch is closed to (a) Write data (b) Read data

Switch is realized with a transistor that has a certain leakage

current i_{leak} , the leads have a certain C_{out}


1° Write data: store "1", apply 3V



to I/O, then open it. What's Q_{cell} ?

$$Q = CV = 50 \times 10^{-15} F \times 3V = 150 fC$$

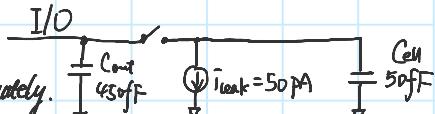2° Storing data; due to leak, charges and voltage will decrease gradually.



How long is it until $V_{cell}(t) = 0.5 V_{cell}(0)$?

$$V(t) = \frac{1}{C_{cell}} \int_0^t i(t) dt + V(0)$$

$$= \frac{1}{50 \text{ fF}} \int_0^t -50 \times 10^{-12} dt + 3$$


$$= -10^3 t + 3$$

$$0.5V(0) = 1.5V$$

$$\therefore t = \frac{1.5}{10^3} = 1.5 \text{ ms}$$

3° Reading data: Assume this is done before any significant leakage

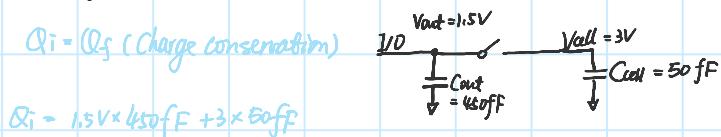happens. I/O is charged to 1.5V before the switch is closed again. What's the voltage change at I/O after the switch is closed?



$$Q_i = Q_f \text{ (charge conservation)}$$

$$Q_i = 1.5V \times 450 \text{ fF} + 3 \times 50 \text{ fF}$$

Charge conservation can only be used when there's no dissipation of charge.

however, energy not conserved in 3°

$$E_i = \frac{1}{2} C_{cell} V_{cell}^2 + \frac{1}{2} C_{load} V_{load}^2 = 731.25 \text{ fJ}$$

$$E_f = \frac{1}{2} (C_{cell} + C_{load}) \cdot V^2 = 680.625 \text{ fJ}$$

∴ a resistor need to be inserted between the switch and C_{cell} .

Probs

Saturday, March 9, 2019 5:33 PM

The voltage across the terminals of a 250 nF capacitor is

$$v = \begin{cases} 50 \text{ V}, & t \leq 0; \\ A_1 e^{-4000t} + A_2 t e^{-4000t} \text{ V}, & t \geq 0, \end{cases}$$

where t is in seconds. The initial current in the capacitor is 400 mA .

Assume the passive sign convention.

(1)

What is the initial energy stored in the capacitor?

Express your answer to three significant figures and include the appropriate units.

► View Available Hint(s)

$$w = 313 \mu\text{J}$$

(2)

Evaluate the coefficient A_1 .

Express your answer to three significant figures and include the appropriate units.

► View Available Hint(s)

$$A_1 = 50.0 \text{ V}$$

(3)

Evaluate the coefficient A_2 .

Express your answer in volts per second using three significant figures.

► View Available Hint(s)

$$A_2 = 1.80 \times 10^6 \text{ V/s}$$

(4)

Select the correct expression for the capacitor current for $t \geq 0$.

► View Available Hint(s)

- $i = (0.4 + 900t)e^{-4000t} \text{ A}$
- $i = (0.4 + 1800t)e^{-4000t} \text{ A}$
- $i = (0.2 - 1800t)e^{-4000t} \text{ A}$
- $i = (0.4 - 900t)e^{-4000t} \text{ A}$
- $i = (0.2 + 1800t)e^{-4000t} \text{ A}$
- $i = (0.4 - 1800t)e^{-4000t} \text{ A}$
- $i = (0.2 + 900t)e^{-4000t} \text{ A}$
- $i = (0.2 - 900t)e^{-4000t} \text{ A}$

(1)

$$W_1 = \frac{1}{2} CV_i^2 = \frac{1}{2} \times 250 \times 10^{-9} \times 50^2 = 3,125 \times 10^{-4} \text{ J}$$

$$(1) W_1 = \frac{1}{2} CV_1^2 = \frac{1}{2} \times 250 \times 10^{-9} \times 50^2 = 3,125 \times 10^{-4} \text{ J}$$

(2)

$$V_0 = 50 \text{ V}$$

$$\therefore A_1 + D = 50$$

$$A_1 = 50 \text{ V}$$

$$(3) i = C \cdot \frac{dv}{dt}$$


$$i_0 = 0.4 = 250 \times 10^{-9} \times (A_1 \times (-4000) + A_2)$$

$$A_2 = 1.8 \times 10^6 \text{ V/s}$$

$$(4) i = C \cdot \frac{dv}{dt}$$

$$= 250 \times 10^{-9} \left[(50 \times (-4000)) + 1.8 \times 10^6 + (-4000) \times 1.8 \times 10^6 t e^{-4000t} \right]$$

$$= (0.4 - 1800t) e^{-4000t}$$

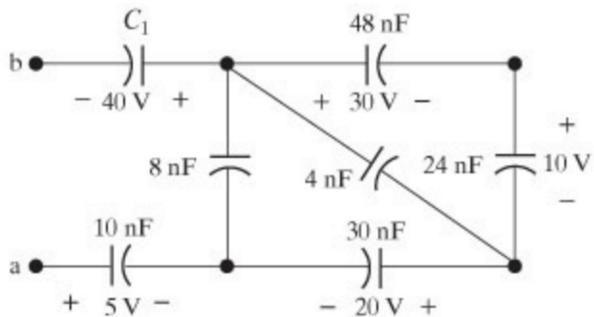

(1)

Find the equivalent capacitance with respect to the terminals a, b for the circuit shown in (Figure 1). Suppose that $C_1 = 19 \text{ nF}$.

Express your answer to three significant figures and include the appropriate units.


$$C_{eq} = 4.94 \text{ nF}$$

(2)

Determine the initial voltage drop for the equivalent capacitance with respect to the terminals a, b for the circuit shown in (Figure 1).

Express your answer to three significant figures and include the appropriate units.


$$V_{0ab} = -15.0 \text{ V}$$

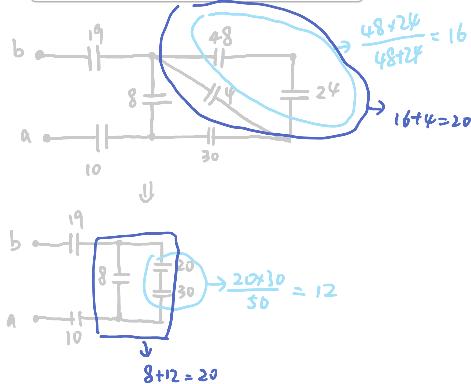

$$C_{eq} = \frac{1}{\frac{1}{20} + \frac{1}{19} + \frac{1}{10}} = 4.94 \text{ nF}$$

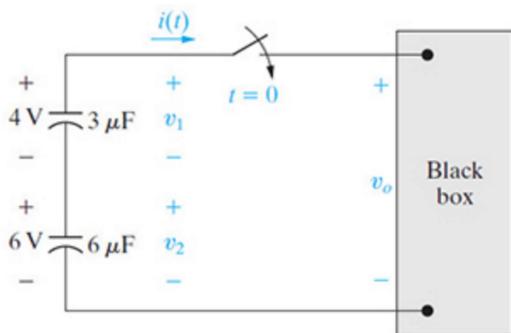(2) Voltage drop : Negative.

~~****~~ $i(t) = 20e^{-t} \mu A$ ($t > 0$)



(1)

Replace the original capacitors with an equivalent capacitor and select the correct expression for $v_o(t)$ for $t \geq 0$.

► [View Available Hint\(s\)](#)

- $v_o(t) = -10e^{-t} - 10 \text{ V}$
- $v_o(t) = -10e^{-t} - 6 \text{ V}$
- $v_o(t) = -10e^{-t} - 4 \text{ V}$
- $v_o(t) = 10e^{-t} \text{ V}$
- $v_o(t) = 10e^{-t} - 6 \text{ V}$
- $v_o(t) = 10e^{-t} - 4 \text{ V}$
- $v_o(t) = 10e^{-t} - 10 \text{ V}$
- $v_o(t) = -10e^{-t} \text{ V}$

(2)

Select the correct expression for $v_1(t)$ for $t \geq 0$.

► [View Available Hint\(s\)](#)

- $v_1(t) = 3.33e^{-t} - 2.67 \text{ V}$
- $v_1(t) = 3.33e^{-t} + 2.67 \text{ V}$
- $v_1(t) = 6.67e^{-t} - 10.67 \text{ V}$
- $v_1(t) = 6.67e^{-t} - 2.67 \text{ V}$
- $v_1(t) = 6.67e^{-t} + 2.67 \text{ V}$
- $v_1(t) = 3.33e^{-t} - 10.67 \text{ V}$
- $v_1(t) = 3.33e^{-t} + 10.67 \text{ V}$
- $v_1(t) = 6.67e^{-t} + 10.67 \text{ V}$

(3)

Select the correct expression for $v_2(t)$ for $t \geq 0$.

► [View Available Hint\(s\)](#)

(3) Select the correct expression for $v_2(t)$ for $t \geq 0$.

► View Available Hint(s)

- $v_2(t) = 6.67e^{-t} + 10.67 \text{ V}$
- $v_2(t) = 3.33e^{-t} + 2.67 \text{ V}$
- $v_2(t) = 6.67e^{-t} - 10.67 \text{ V}$
- $v_2(t) = 3.33e^{-t} + 10.67 \text{ V}$
- $v_2(t) = 6.67e^{-t} + 2.67 \text{ V}$
- $v_2(t) = 6.67e^{-t} - 2.67 \text{ V}$
- $v_2(t) = 3.33e^{-t} - 10.67 \text{ V}$
- $v_2(t) = 3.33e^{-t} - 2.67 \text{ V}$

(4)

How much energy is delivered to the black box in the time interval $0 \leq t < \infty$?

Express your answer to three significant figures and include the appropriate units.

► View Available Hint(s)

$$w_{\text{delivered}} = 100 \mu\text{J}$$

(5)

How much energy was initially stored in the series capacitors?

Express your answer to three significant figures and include the appropriate units.

► View Available Hint(s)

$$w_{\text{initial}} = 132 \mu\text{J}$$

(6)

How much energy is trapped in the ideal capacitors?

Express your answer to three significant figures and include the appropriate units.

► View Available Hint(s)

$$w_{\text{trapped}} = 32.0 \mu\text{J}$$

$$(1) C_{\text{eq}} = \frac{3 \times 6}{9} = 2 \mu\text{F}$$

$$\begin{aligned} V_o &= -\frac{1}{C_{\text{eq}}} \int_0^t 20e^{-t} dt + 10 \\ &\text{because current direction} \end{aligned}$$

$$\begin{aligned} &= 10e^{-t} \Big|_0^t + 10 \\ &= 10e^{-t} \end{aligned}$$

(2)

$$V_i = -\frac{1}{C} \int_0^t 20e^{-t} dt + 3$$

$$= 6.67 e^{-t} - 2.67 \text{ V}$$

$$\begin{aligned}
 & G_1 J_1 = 6.67 e^{-t} - 2.67 \text{ V} \\
 & \triangle \quad W_{\text{delivered}} = \int_0^{\infty} iV dt = \int_0^{\infty} 10e^{-t} \cdot 20e^{-t} dt \\
 & \qquad \qquad \qquad \downarrow \text{mA} \\
 & = \int_0^{\infty} 200e^{-2t} dt \\
 & = -100e^{-2t} \Big|_0^{\infty} \\
 & = 100 \text{ J}
 \end{aligned}$$

$$\begin{aligned}
 (5) \quad W &= \frac{1}{2} CV^2 = \frac{1}{2} (3 \times 4^2 + 6 \times 6^2) \\
 &= 132 \text{ J}
 \end{aligned}$$

$$(6) \quad 132 - 100 = 32 \text{ J}$$